



## INDEX PAGE



Sr. No.	Name of the Experiment	Page No.	Date of Performance	Sign of Teacher & Date	Remark
0)	Study of different electronic components		26-03-21		
1)	Observe and draw V-I characteristics of PN Diode & LED diode		26-03-21		
2)	Observe and draw the V-I characteristics and regulation characteristics of zener diode		05-03-21		
3)	Design clipper circuit using diode		19-03-21		
4)	Design clamper circuit using diode		19-03-21		
5)	Obtain ripple factor of half wave rectifier circuit with and without filter		12-03-21		
6)	Draw the input and output characteristics of a transistor connected in CE configuration		12-03-21		
7)	Design bipolar junction transistor as a switch		09-04-21		
8)	open ended experiment		09-04-21		