

[Total No. of Questions: 5] Seat No

[Total No of Pages: 2]

G. H. Raisonni of Engineering and Management, Pune.
(An Autonomous Institution affiliated to Savitribai Phule, Pune University)
F. Y. B .Tech (Term -I) (AI/COMP/DS/IT)
ESE Winter – 2020 (2020 Pattern)
Introduction to Discrete Devices and circuits (UECL105)

[Time: 2 Hours]

[Max. Marks: 50]

Course Outcome

CO1: Relate operation of diodes, types of diodes and their role in design of simple electronic applications.

CO2: Develop the capability to analyze and design simple circuits containing non-linear elements such as transistors using the concepts of load lines, operating points for various biasing methods.

CO3: Classify Power amplifiers, Oscillators & Display Devices.


CO4: Interpret the operation of the Field Effect Transistor (FET), Metal Oxide Semiconductor Field Effect Transistor (MOSFET) and design FET circuits

CO5: Demonstrate familiarity with basic electronic components and use them to design simple electronic circuits

Instructions to the candidates:

- 1) All questions compulsory**
- 2) Neat diagrams must be drawn wherever necessary.**
- 3) Figures to the right indicate full marks.**
- 4) Assume suitable data, if necessary.**

- | | | | | |
|-----|----|--|-----|----|
| CO1 | a) | Draw and explain Clippers and Clampers circuits. | [5] | L1 |
| | b) | The applied input a.c. power to a half-wave rectifier is 100 watts. The d.c. output power obtained is 40 watts.
(i) What is the rectification efficiency ?
(ii) What happens to remaining 60 watts ? | [5] | L5 |
| CO2 | a) | Draw the CC configuration of BJT and explain its input and output characteristics. | [5] | L4 |
| | b) | A common base transistor amplifier has an input resistance of $20\ \Omega$ and output resistance of $100\ k\Omega$. The collector load is $1\ k\Omega$. If a signal of $500\ mV$ is applied between emitter and base, find the voltage amplification. Assume α_{ac} to be nearly one. | [5] | L4 |

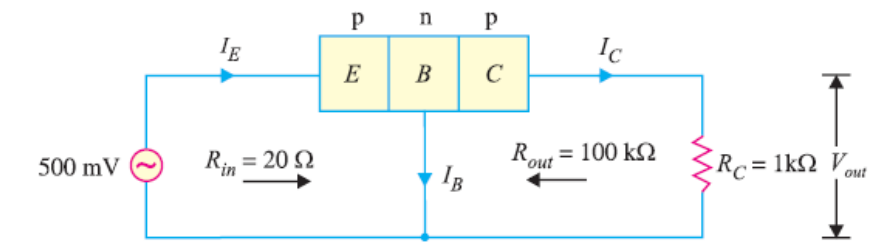

- CO3 a) Draw the CE circuit and explain the DC load line and importance of Q point [5] L4
- b) Explain on brief feedback Amplifier. [5] L2
- CO4 a) What is Pinch off voltage? Explain its significance. [5] L4
- b) Draw the diagram of D-MOSFET and explain its working and characteristics. [5] L4
- CO5 a) Explain the working of passive sensors with proper example. [5] L2
- b) Design the simple electronic circuit to measure the temperature of body and display in Digital format. [5] L6

