

[Total No. of Questions: 2] Seat No

[Total No of Pages: 1]

G. H. Rasoni of Engineering and Management, Pune.

(An Autonomous Institution)

F. Y. B .Tech (Term- I)

CAE II- 2020(2020 Pattern)

Introduction to Discrete Devices (UECL105)

[Time: 1 Hours]

[Max. Marks: 15]

**Course Outcome**

**CO1: Relate operation of diodes, types of diodes and their role in design of simple electronic applications.**

**CO2: Develop the capability to analyze and design simple circuits containing non-linear elements such as transistors using the concepts of load lines, operating points for various biasing methods.**

**CO3: Classify Power amplifiers, Oscillators & Display Devices.**

**CO4: Interpret the operation of the Field Effect Transistor (FET), Metal Oxide Semiconductor Field Effect Transistor (MOSFET) and design FET circuits**

**CO5: Demonstrate familiarity with basic electronic components and use them to design simple electronic circuits.**

Instructions to the candidates:

- 1) All questions compulsory
- 2) Neat diagrams must be drawn wherever necessary.
- 3) Figures to the right indicate full marks.
- 4) Assume suitable data, if necessary.

CO2 a) What is BJT and explain its different types with symbol and structure. [3]

b) Design single stage CE amplifier and explain in details. [5]

CO3 a) Explain the following terms in details [3]

- 1) Gain of BJT
- 2) Stability factor
- 3) Need of Stabilization

b) Define DC load line with proper circuit diagram and explain Q-Point. [4]

\*\*\*\*\*All the best\*\*\*\*\*

