
Boolean Algebra

Boolean Algebra Summary

- We can interpret high or low voltage as representing true or false.
- A variable whose value can be either 1 or 0 is called a Boolean variable.
- AND, OR, and NOT are the basic Boolean operations.
- We can express Boolean functions with either an expression or a truth table.
- Every Boolean expression can be converted to a circuit.
- Now, we'll look at how Boolean algebra can help simplify expressions, which in turn will lead to simpler circuits.

Boolean Algebra Summary

- Recall that the two binary values have different names:
 - True/False
 - On/Off
 - Yes/No
 - 1/0
- We use 1 and 0 to denote the two values.
- The three basic logical operations are:
 - AND
 - OR
 - NOT
- AND is denoted by a dot (\cdot).
- OR is denoted by a plus ($+$).
- NOT is denoted by an overbar ($\bar{}$), a single quote mark ($'$) after, or (\sim) before the variable

Boolean Algebra Summary

- Examples:

- is read "Y is equal to A AND B."
- is read "z is equal to x OR y."
- is read "X is equal to NOT A."

Tabular listing of the values of a function for all possible combinations of values on its arguments

Example: Truth tables for the basic logic operations:

AND		
X	Y	$Z = X \cdot Y$
0	0	0
0	1	0
1	0	0
1	1	1

OR		
X	Y	$Z = X + Y$
0	0	0
0	1	1
1	0	1
1	1	1

NOT	
X	$Z = \bar{X}$
0	1
1	0

Boolean Operator Precedence

- The order of evaluation is:
 1. Parentheses
 2. NOT
 3. AND
 4. OR
- Consequence: Parentheses appear around OR expressions
- Example: $F = A(B + C)(C + D)$

Boolean Algebra Postulates

- Commutative Law

$$x \cdot y = y \cdot x$$

$$x + y = y + x$$

- Identity Element

$$x \cdot 1 = x$$

$$x + 0 = x$$

$$x' \cdot 1 = x'$$

$$x' + 0 = x'$$

- Complement

$$x \cdot x' = 0$$

$$x + x' = 1$$



Boolean Algebra Theorems

Theorem 1

- $x \cdot x = x$

$x + x = x$

• Theorem 2

- $x \cdot 0 = 0$

$x + 1 = 1$

• Theorem 3: *Involution*

- $(x')' = x$

$(\overline{\overline{x}}) = x$



Boolean Algebra Theorems

- Theorem 4:

- *Associative:* $(x \cdot y) \cdot z = x \cdot (y \cdot z)$
 $(x + y) + z = x + (y + z)$

- *Distributive :*

$$x \cdot (y + z) = (x \cdot y) + (x \cdot z)$$

$$x + (y \cdot z) = (x + y) \cdot (x + z)$$

- Theorem 5: *DeMorgan*

- $(x \cdot y)' = x' + y'$ $(x + y)' = x' \cdot y'$

- $\overline{x \cdot y} = \bar{x} + \bar{y}$ $\overline{x + y} = \bar{x} \cdot \bar{y}$

- Theorem 6: *Absorption*

- $x \cdot (x + y) = x$ $x + (x \cdot y) = x$



Truth Table to Verify DeMorgan's

$$\overline{X + Y} = \overline{X} \cdot \overline{Y}$$

$$\overline{X \cdot Y} = \overline{X} + \overline{Y}$$

X	Y	$X \cdot Y$	$X + Y$	\overline{X}	\overline{Y}	$\overline{X + Y}$	$\overline{X} \cdot \overline{Y}$	$\overline{X \cdot Y}$	$\overline{X} + \overline{Y}$
0	0	0	0	1	1	1	1	1	1
0	1	0	1	1	0	0	0	1	1
1	0	0	1	0	1	0	0	1	1
1	1	1	1	0	0	0	0	0	0

- Generalized DeMorgan's Theorem:

$$\overline{X_1 + X_2 + \dots + X_n} = \overline{X_1} \cdot \overline{X_2} \cdot \dots \cdot \overline{X_n}$$




$$\overline{X_1 \cdot X_2 \cdot \dots \cdot X_n} = \overline{X_1} + \overline{X_2} + \dots + \overline{X_n}$$

Logic Gates

- In the earliest computers, switches were opened and closed by magnetic fields produced by energizing coils in *relays*. The switches in turn opened and closed the current paths.
- Later, *vacuum tubes* that open and close current paths electronically replaced relays.
- Today, *transistors* are used as electronic switches that open and close current paths.


Logic Gate Symbols

- Logic gates have special symbols:

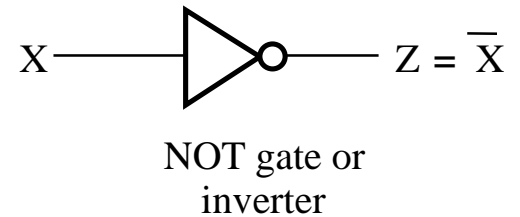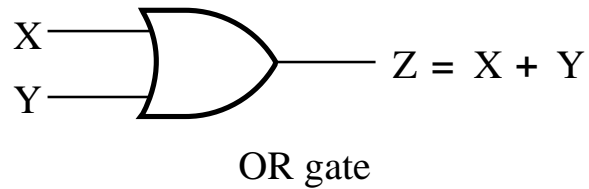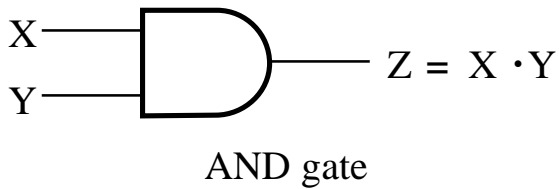

Boolean Functions

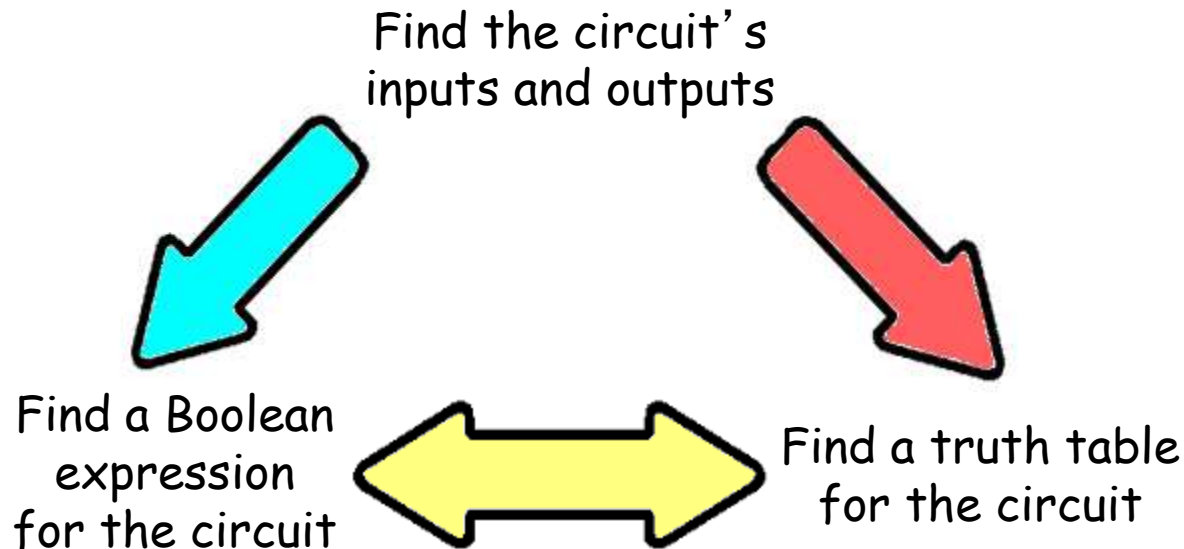- A **Boolean function** is a function whose arguments, as well as the function itself, assume values from a two-element set ($\{0, 1\}$).
- **Example:** $F(x, y) = x' y' + x y z + x' y$
- After finding the circuit inputs and outputs, you can come up with either an expression or a truth table to describe what the circuit does.
- You can easily convert between expressions and truth tables.



Boolean Functions


- **Boolean Expression/Function**

Example: $F(x, y) = x + y'z$

- **Truth Table**

All possible combinations
of input variables

- **Logic Circuit**

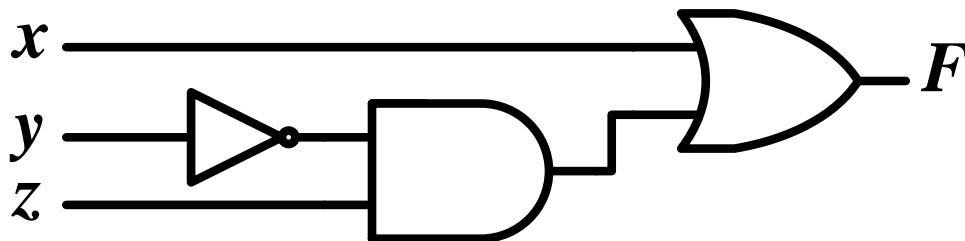

x	y	z	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

Logic Diagrams and Expressions


Truth Table

X Y Z	$F = X + \bar{Y} \times Z$
0 0 0	0
0 0 1	1
0 1 0	0
0 1 1	0
1 0 0	1
1 0 1	1
1 1 0	1
1 1 1	1

Logic Equation/Boolean Function

$$F = X + \bar{Y} Z$$

Logic Circuit

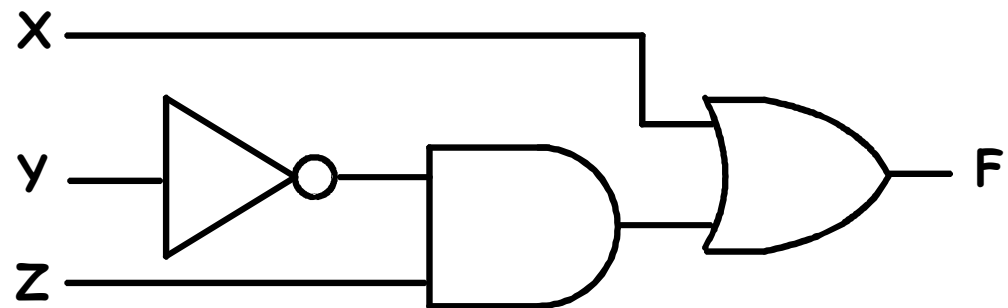

- Boolean equations, truth tables and logic diagrams describe the same function!
- Truth tables are unique, but expressions and logic diagrams are not. This gives flexibility in implementing functions.

Boolean Functions Exercise

- The truth table for the function:

$$F(X, Y, Z) = XY + \bar{Y}Z \text{ is:}$$

X	Y	Z	XY	\bar{Y}	$\bar{Y}Z$	$F = XY + \bar{Y}Z$
0	0	0	0	1	0	0
0	0	1	0	1	1	1
0	1	0	0	0	0	0
0	1	1	0	0	0	0
1	0	0	0	1	0	0
1	0	1	0	1	1	1
1	1	0	1	0	0	1
1	1	1	1	0	0	1

Draw the logic circuit for the boolean function above.

Converting from Truth Table to Boolean Function

- In designing digital circuits, the designer often begins with a truth table describing what the circuit should do.
- The design task is largely to determine what type of circuit will perform the function described in the truth table.
- While some people seem to have a natural ability to look at a truth table and immediately envision the necessary logic gate or relay logic circuitry for the task, there are procedural techniques available for the rest of us.
- Here, Boolean algebra proves its utility in a most dramatic way!

Converting from Truth Table to Boolean Function

- This problem will be solved by showing that any Boolean function can be represented by a Boolean sum of Boolean products of the variables and their complements or the product of sums.
- There are two ways to convert from truth tables to Boolean functions:
 1. Using Sum of Products /Minterms
 2. Using Product of Sums /Maxterms

Converting from Truth Table to Boolean Function

• Minterm

- Product (*AND* function)
- Contains all variables
- Evaluates to '1' for a specific combination

Example

$$\begin{array}{l} A = 0 \\ B = 0 \\ C = 0 \end{array} \left\{ \begin{array}{l} \bar{A} \\ (\bar{0}) \\ \downarrow \\ 1 \end{array} \right. \cdot \left\{ \begin{array}{l} \bar{B} \\ (\bar{0}) \\ \downarrow \\ 1 \end{array} \right. \cdot \left\{ \begin{array}{l} \bar{C} \\ (\bar{0}) \\ \downarrow \\ 1 \end{array} \right. = 1$$

	A	B	C	Minterm	
0	0	0	0	m_0	$\bar{A} \bar{B} \bar{C}$
1	0	0	1	m_1	$\bar{A} \bar{B} C$
2	0	1	0	m_2	$\bar{A} B \bar{C}$
3	0	1	1	m_3	$\bar{A} B C$
4	1	0	0	m_4	$A \bar{B} \bar{C}$
5	1	0	1	m_5	$A \bar{B} C$
6	1	1	0	m_6	$A B \bar{C}$
7	1	1	1	m_7	$A B C$

Converting from Truth Table to Boolean Function

• Maxterm

- Sum (OR function)
- Contains all variables
- Evaluates to '0' for a specific combination

Example

$$\begin{array}{l} A = 1 \\ B = 1 \\ C = 1 \end{array} \left. \vphantom{\begin{array}{l} A = 1 \\ B = 1 \\ C = 1 \end{array}} \right\} \begin{array}{ccc} \bar{A} & \bar{B} & \bar{C} \\ (\bar{1}) & (\bar{1}) & (\bar{1}) \\ \downarrow & \downarrow & \downarrow \\ 0 & \cdot & 0 \cdot 0 = 0 \end{array}$$


	A B C	Maxterm	
0	0 0 0	M_0	$A + B + C$
1	0 0 1	M_1	$A + B + \bar{C}$
2	0 1 0	M_2	$A + \bar{B} + C$
3	0 1 1	M_3	$A + \bar{B} + \bar{C}$
4	1 0 0	M_4	$\bar{A} + B + C$
5	1 0 1	M_5	$\bar{A} + B + \bar{C}$
6	1 1 0	M_6	$\bar{A} + \bar{B} + C$
7	1 1 1	M_7	$\bar{A} + \bar{B} + \bar{C}$

Converting from Truth Table to Boolean Function

- Truth Table to Boolean Function

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	1
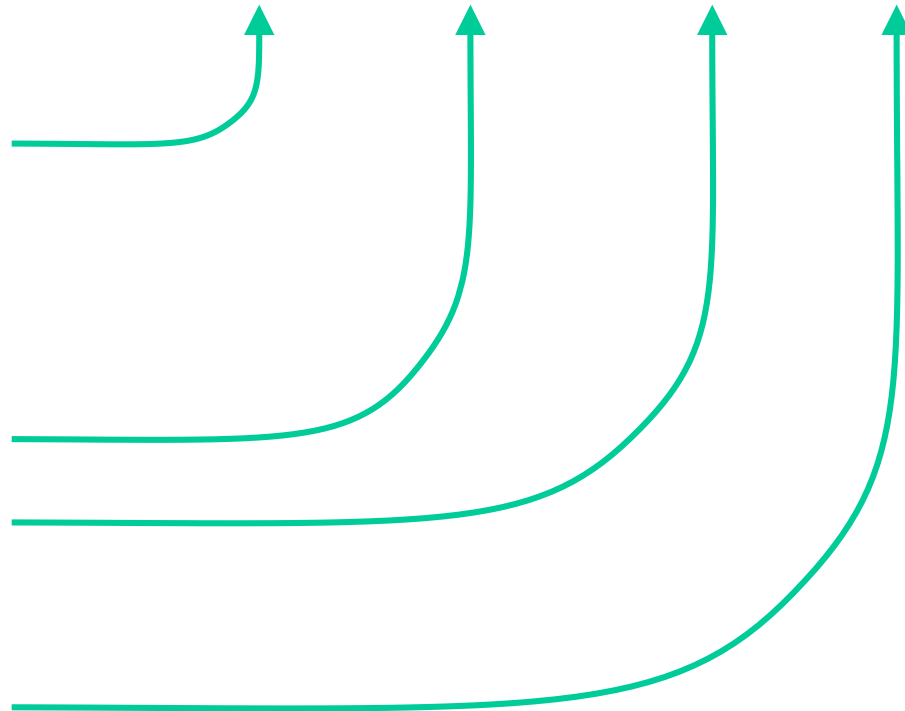
$$F = \overline{A}\overline{B}C + \overline{A}\overline{B}\overline{C} + \overline{A}BC + ABC$$



Using Minterms

Converting from Truth Table to Boolean Function

- Truth Table to Boolean Function

$$F = (A + B + C)(A + \bar{B} + C)(A + \bar{B} + \bar{C})(\bar{A} + \bar{B} + C)$$

A	B	C	\bar{F}
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	0

Using Maxterms

Converting from Truth Table to Boolean Function

- Sum of *Minterms*

$$F = \overline{A}\overline{B}C + \overline{A}B\overline{C} + A\overline{B}\overline{C} + ABC$$

$$F = m_1 + m_4 + m_5 + m_7$$

$$F = \sum (1,4,5,7)$$

- Product of *Maxterms*

$$\overline{F} = \overline{A}\overline{B}\overline{C} + \overline{A}B\overline{C} + A\overline{B}\overline{C} + ABC$$

$$\overline{\overline{F}} = \overline{\overline{A}\overline{B}\overline{C} + \overline{A}B\overline{C} + A\overline{B}\overline{C} + ABC}$$

$$F = \overline{\overline{A}\overline{B}\overline{C}} \cdot \overline{\overline{A}B\overline{C}} \cdot \overline{A\overline{B}\overline{C}} \cdot \overline{ABC}$$

$$F = (A + B + C)(A + \overline{B} + C)(A + \overline{B} + \overline{C})(\overline{A} + \overline{B} + C)$$

$$F = M_0 \quad M_2 \quad M_3 \quad M_6$$

$$F = \prod (0,2,3,6)$$

	A	B	C	F	\overline{F}
0	0	0	0	0	1
1	0	0	1	1	0
2	0	1	0	0	1
3	0	1	1	0	1
4	1	0	0	1	0
5	1	0	1	1	0
6	1	1	0	0	1
7	1	1	1	1	0