

## OPEN ENDED EXPERIMENT

## EXPERIMENT NO. : 8

**Aim:** To set up a transistor series regulator.

**Equipment:** Multisim Software, variable supply, resistor, transistor, zener voltage, current.

**Theory:** The output voltage of a practical power supply changes with load current, generally dropping as load current increases. The power supply specifications include a full load current rating, which is the maximum current that can be drawn from the supply.

The terminal voltage when full load current is drawn is called the full load voltage (VFL). The no load voltage (VNL) is the terminal voltage when zero current is drawn from the supply, that is the open circuit terminal voltage.

An irregular/unregulated power supply has poor regulation i.e., output voltage changes with load variations. If a power supply does have poor regulation it poses high internal impedance. A simple emitter follower regulator. It is also called as series regulator since the control element is in series with the load. It is also called as the pass transistor because it conducts or passes all the load current through the regulator. It is usually a power transistor. The zener provides the voltage reference, and base to emitter,

voltage to the transistor is the control voltage.


The value of  $R_s$  current must be sufficiently small, to keep the zener in its reverse breakdown region.

Writing Kirchhoff's voltage law to output circuit.

$$V_o + V_{BE} - V_z = 0$$

$$\therefore, V_{BE} = V_z - V_o.$$

### Circuit Diagram of Series Regulators

 

If  $V_z$  is perfectly constant, the above equation is valid at all times, and any change in  $V_o$  must cause change in  $V_{BE}$ , in order to maintain equality.

When current demand is increased by decreasing  $R_L$ ,  $V_o$  tends to decrease. This will increase.



The forward bias of the transistor thereby increasing level of conduction. Thus, the output current is increased to keep  $I_L R_L$  a constant. The reverse process occurs when  $R_L$  is increased. Thus, the above circuit keeps the output voltage constant even if the load varies widely.

### Procedure:


- 1.) Draw the same circuit on the breadboard OR multisim as shown in figure above.
- 2.) Keep the input voltage constant at  $V_{in}$ , i.e. 10V.
- 3.) Vary the load resistance.
- 4.) Draw the Plot between  $I_L$  and  $V_o$ .

### Observation:

Sr No.	$V_o$	$I_L$
1.	1.3 V	15 A m p
2.	566 mV	5 A m p
3.	677 mV	7 A m p

Conclusion: From the above experiment we can eventually conclude that we have eventually conclude that we have has about  $I_L$  and  $V_o$  Relation & their Plot.

### Line Regulation

 

### Load Regulation

