

[Total No. of Questions: 2] Seat No  [Total No of Pages: 1]

G. H. Rasoni of Engineering and Management, Pune.

(An Autonomous Institution)

F. Y. B .Tech (Term- I)

CAE I- 2020(2020 Pattern)

Introduction to Discrete Devices (UECL105)

[Time: 1 Hours]

[Max. Marks: 15]

**Course Outcome**

**CO1: Relate operation of diodes, types of diodes and their role in design of simple electronic applications.**

**CO2: Develop the capability to analyze and design simple circuits containing non-linear elements such as transistors using the concepts of load lines, operating points for various biasing methods.**

**CO3: Classify Power amplifiers, Oscillators & Display Devices.**

**CO4: Interpret the operation of the Field Effect Transistor (FET), Metal Oxide Semiconductor Field Effect Transistor (MOSFET) and design FET circuits**

**CO5: Demonstrate familiarity with basic electronic components and use them to design simple electronic circuits.** Instructions to the candidates:

- 1) All questions compulsory
- 2) Neat diagrams must be drawn wherever necessary.
- 3) Figures to the right indicate full marks.
- 4) Assume suitable data, if necessary.

- |     |  |     |
|-----|--|-----|
| CO1 | a) Define rectifier and Explain the Half wave rectifier with waveform  | [3] |
|     | b) Define the clipper and explain parallel negative clipper in details.  | [3] |
| CO2 | a) What is the necessary AC input power from transformer secondary used in a HWR to deliver 700W of DC power to load? What would be the input AC power for the same load in Full wave rectifier? | [4] |

**OR**

- |    |   |     |
|----|---|-----|
| b) | For Half wave rectifier peak voltage is 32.53V, the diode forward resistance is 15 $\Omega$ and resistance secondary winding is 10 $\Omega$ . For a load resistance of 4K $\Omega$ , Calculate average, rms values of load current and voltage, rectification efficiency & ripple factor. | [4] |
| c) | Explain the working Bridge rectifier with its waveform also explain the efficiency and ripple factor of Bridge rectifier.   | [5] |

\*\*\*\*\*All the best\*\*\*\*\*